

4-22 What is the range of the gain  $v_O/v_S$  in Figure P4-22?

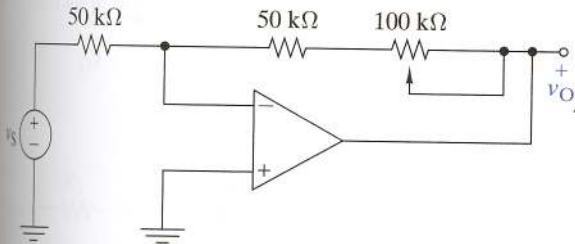


FIGURE P 4 - 22

- 4-23 (a) Find  $v_O$  in terms of  $v_S$  in Figure P4-23.  
(b) Find  $i_O$  for  $v_S = 1.5$  V.

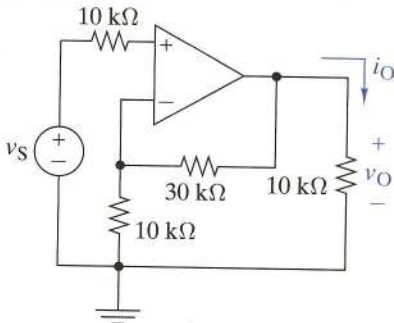


FIGURE P4-23

4-25 What is the gain  $v_O/v_S$  in Figure P4-25 when the switch is in position 1? Repeat for positions 2 and 3.

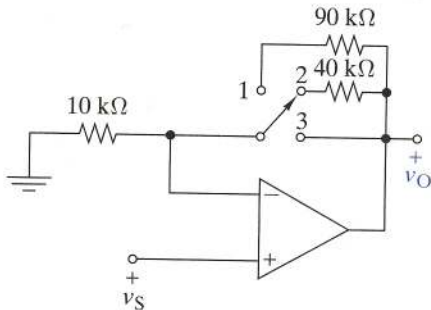


FIGURE P4 - 25

4-26 Find  $v_O$  in terms of the inputs  $v_1$  and  $v_2$  in Figure P4-26.

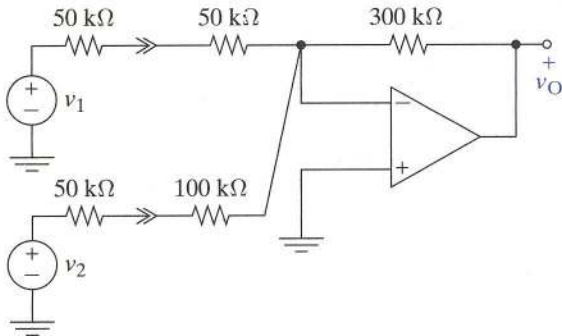


FIGURE P4-26

4-30 Find  $v_O$  in terms of the inputs  $v_{S1}$  and  $v_{S2}$  in Figure P4-30

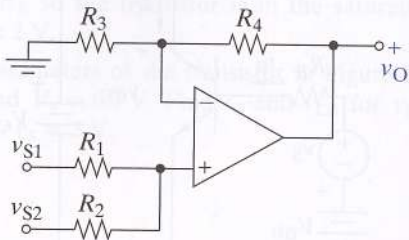


FIGURE P4 - 30

4-34 Use node-voltage analysis in Figure P4-34 to show that  $i_O = -v_S/2R$  regardless of the load. That is, show that the circuit is a voltage-controlled current source.

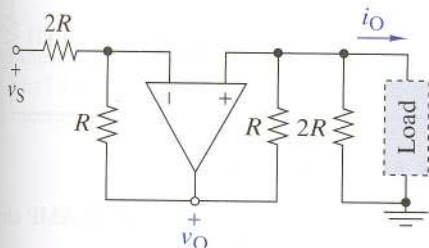


FIGURE P4-34

4-36 Find  $v_O$  in terms of the inputs  $v_{S1}$  and  $v_{S2}$  in Figure P4-36.


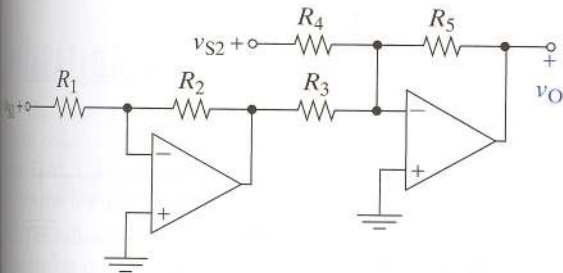


FIGURE P 4 - 36

**4–37** Find the output  $v_2$  in terms of the input  $v_1$  in Figure P4–37.

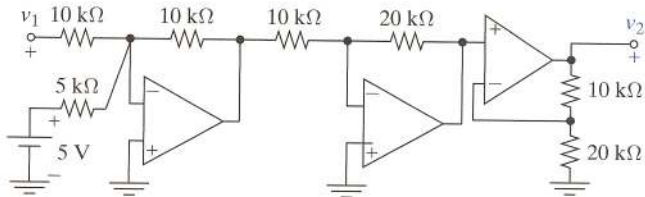

**FIGURE P4–37**



4-47 **D** Design the interface circuit in Figure P4-47 so that the output is  $v_2 = (50v_1 + 3) \text{ V}$ .

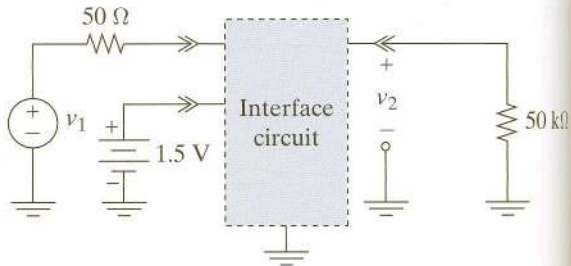


FIGURE P4-47

**4–55 D** A medical-grade pressure transducer has been developed for use in invasive blood pressure monitoring. The output voltage of the transducer is  $v_{TR} = (0.05P - 0.75)$  mV, where  $P$  is pressure in mmHg. The output resistance of the transducer is  $300\Omega$ . The blood pressure measurement is to be an input to an existing multisensor monitoring system. This system treats a 1-V input as a blood pressure of 20 mmHg and a 10-V input as 200 mmHg. Design an OP AMP circuit to interface the new pressure transducer with the existing monitoring system.