

11-5 Find the voltage transfer function $T_V(s) = V_2(s)/V_1(s)$ in Figure P11-5.

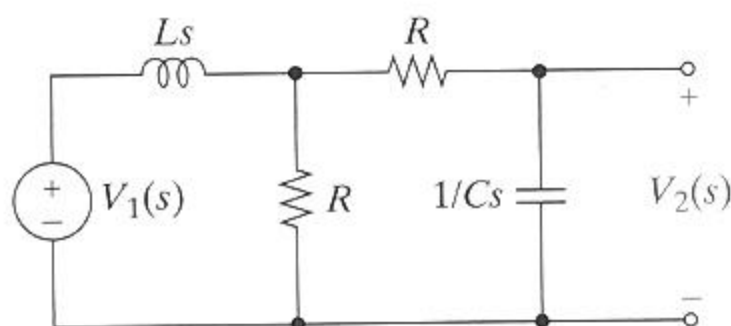


FIGURE P11-5

11-8 Find the current transfer function $T_I(s) = I_2(s)/I_1(s)$ in Figure P11-8. Select values of R and L so that $T_I(s)$ has a pole at $s = -500$ rad/s.

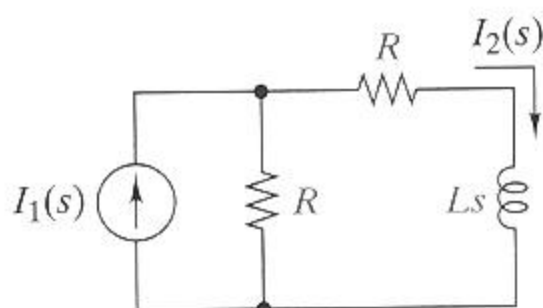


FIGURE P11-8

11-9 Find the voltage transfer function $T_V(s) = V_2(s)/V_1(s)$ of the cascade connection in Figure P11-9. Locate the poles and zeros of the transfer function.

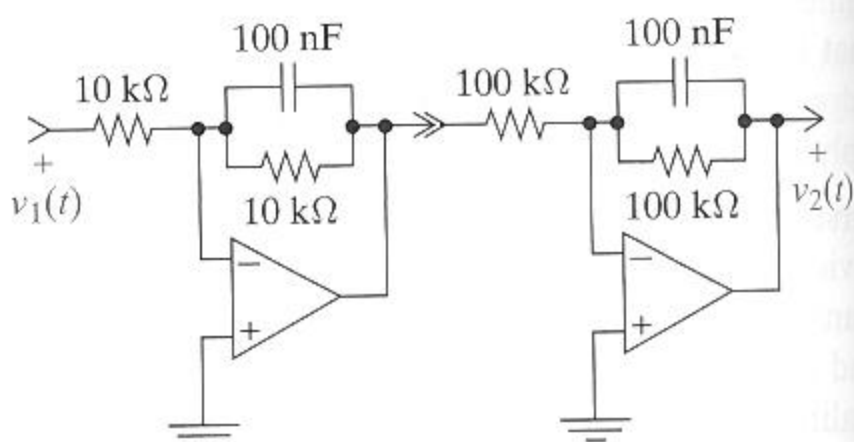


FIGURE P11-9

11-30 The circuit in Figure P11-30 is in the steady state with $i_1(t) = 10 \cos 5000t$ mA. Find the steady-state voltage $v_{2ss}(t)$. Repeat with $i_1(t) = 5 \cos 2500t$ mA.

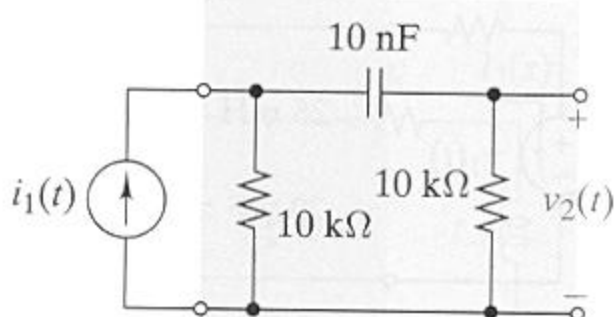


FIGURE P11-30

- Design a circuit that realizes a given $T(s)$ and meets other stated constraints.
- Evaluate alternative designs using stated criteria.

-51 **D** Design a circuit to realize the transfer function below using only resistors, capacitors, and OP AMPs. Scale the circuit so that all resistors are greater than $10\text{ k}\Omega$ and all capacitors are less than $1\text{ }\mu\text{F}$.

$$T_V(s) = \pm \frac{2 \times 10^4}{(s + 250)(s + 2500)}$$

-52 **D** Design a circuit to realize the transfer function below using only resistors, capacitors, and not more than one OP AMP. Scale the circuit so that all capacitors are exactly 10 nF .

$$T_V(s) = \pm \frac{100(s + 1000)}{(s + 250)(s + 2000)}$$

12-3 Find the transfer function $T_V(s) = V_2(s)/V_1(s)$ of the circuit in Figure P12-3.

- (a) Find the dc gain, infinite frequency gain, and cutoff frequency. Identify the type of gain response.
- (b) Sketch the straight-line approximation of the gain response.
- (c) What element values would you change to increase the passband gain to 10?

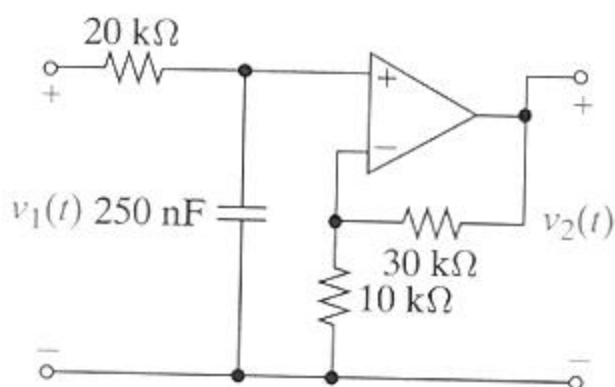


FIGURE P12-3

12-9 The transfer function of a first-order circuit is

$$T(s) = \frac{2}{10^{-2} + 20/s}$$

- (a) Identify the type of gain response. Find the cutoff frequency and the passband gain.
- (b) Sketch the straight-line gain response. Use the straight-line gain to estimate the gain at $\omega = 0.5\omega_C$, ω_C , and $2\omega_C$.

12-16 The circuit in Figure P12-16 produces a bandstop response for a suitable choice of element values. Identify the elements that control the two cutoff frequencies. Select the element values so that the cutoff frequencies are 10 rad/s and 500 rad/s. What is the passband gain for your choices? Use practical element values with $R \geq 10 \text{ k}\Omega$, $L \leq 100 \text{ mH}$, and $C \leq 1 \text{ }\mu\text{F}$.

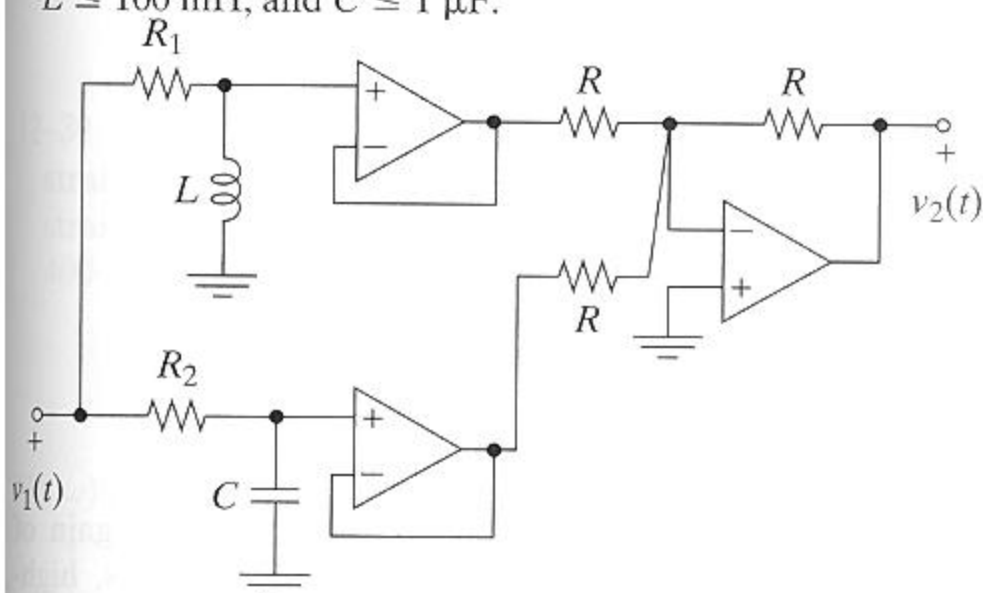


FIGURE P 1 2 - 1 6

12-55 Design Evaluation

Your company issued a request for proposals listing the following design requirements and evaluation criteria.

Design requirements: Design a low-pass filter with a pass-band gain of $9 \pm 10\%$ and a cutoff frequency of $90 \pm 10\%$ krad/s. The filter input is driven by a sensor with a $1\text{-k}\Omega$ source resistance and an open-circuit voltage range of $\pm 1.6\text{ V}$.

Evaluation criteria: Evaluate filter performance, parts count, use of standard parts, and cost. The two vendors have responded with the designs shown in Figure P12-55. As a junior engineer, you are asked to evaluate the designs and recommend a vendor. Which vendor would you recommend and why?

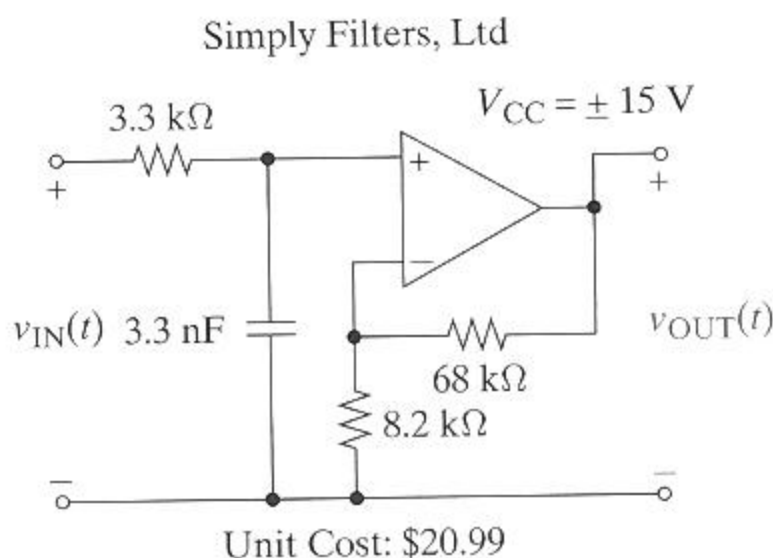
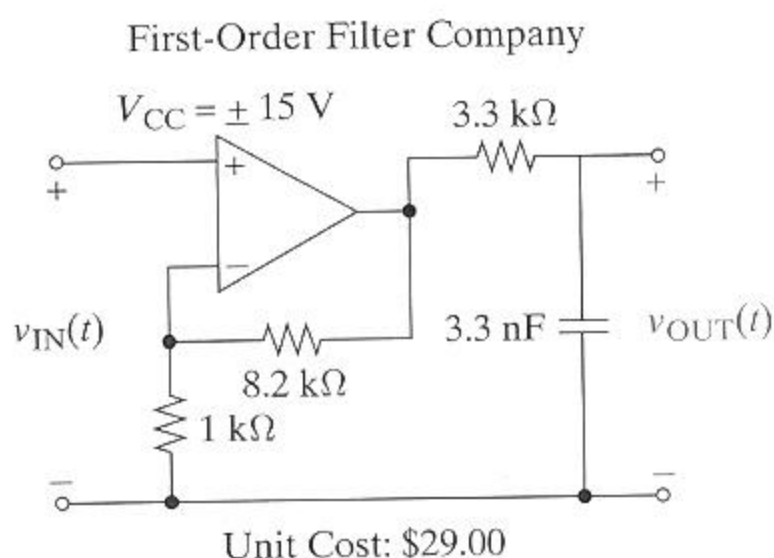


FIGURE P12-55