

3-15(a) Formulate mesh-current equations for the circuit in Figure P3-15.

(b) Formulate node-voltage equations for the circuit in Figure P3-15.

(c) Which set of equations would be easier to solve? Why?

(d) Find v_x and i_x using whichever method you prefer.

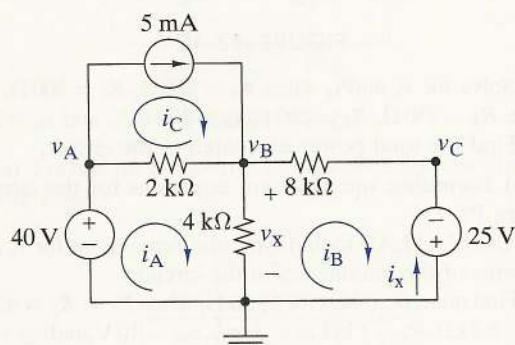


FIGURE P3-15

3-16 Use mesh-current equations, node-voltage equations, or simple engineering intuition to find the input resistance of the circuit in Figure P3-16.

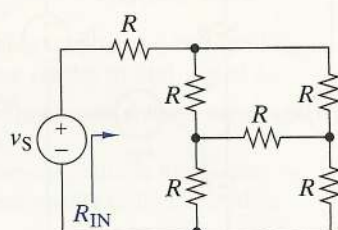


FIGURE P3-16

3-17 In Figure P3-17 all of the resistors are $1\text{ k}\Omega$ and $v_S = 10\text{ V}$. The voltage at node C is found to be $v_C = -2\text{ V}$ when node B is connected to ground. Find the node voltages v_A and v_D , and the mesh currents i_A and i_B .

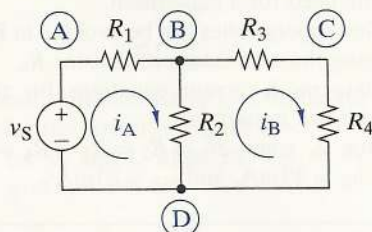


FIGURE P3-17

3-18 Use Figure P3-17 and MATLAB to solve the following problems:

- Using mesh-current analysis, find a symbolic expression for i_A in terms of the circuit parameters.
- Compute the ratio v_S/i_A .

(c) Find a symbolic expression for the equivalent resistance of the circuit by combining resistors in series and parallel. Compare your answer to the results from part (b).

3-19 Use OrCAD to find the node voltages v_A and v_B and the mesh currents i_A , i_B , and i_C in Figure P3-19.

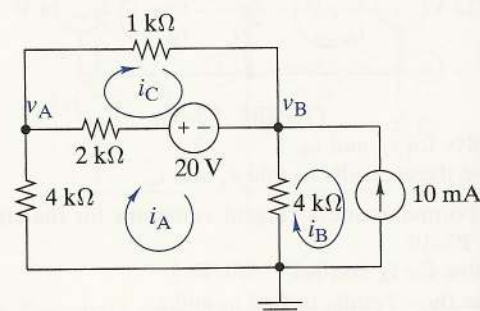


FIGURE P3-19

3-20(a) Use MATLAB and mesh-current analysis to solve for the mesh currents i_A , i_B , i_C , and i_D in Figure P3-20.

(b) Solve for the same currents using node-voltage analysis and compare the effort required with each technique.

(c) Use OrCAD to verify your results in the previous two parts.

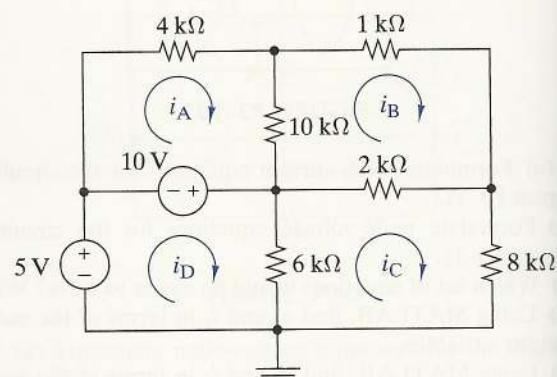


FIGURE P3-20

OBJECTIVE 3-2 LINEARITY PROPERTIES (SECT. 3-3)

- Given a circuit containing linear resistors and one independent source, use the proportionality principle to find selected signal variables.
- Given a circuit containing linear resistors and two or more independent sources, use the superposition principle to find selected signal variables.

See Examples 3-10, 3-11, 3-12 and Exercises 3-18, 3-19, 3-21, 3-22

- 3-21 Find the proportionality constant $K = v_O/i_S$ for the circuit in Figure P3-21.

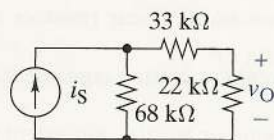


FIGURE P3-21

- 3-22 Find the proportionality constant $K = i_O/i_S$ for the circuit in Figure P3-22.

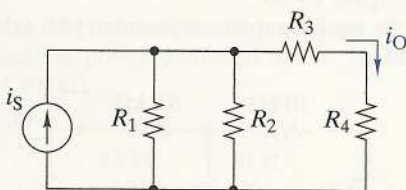


FIGURE P3-22

- 3-23 Find the proportionality constant $K = v_O/v_S$ for the circuit in Figure P3-23.

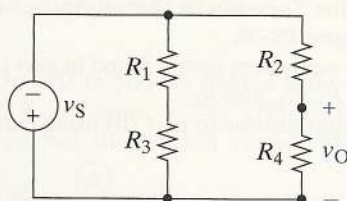


FIGURE P3-23

- 3-24 Use the unit output method to find v_O in Figure P3-24.

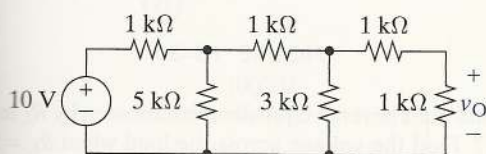


FIGURE P3-24

- 3-25 Use the unit output method to find i_O in Figure P3-25.

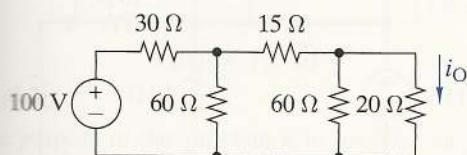


FIGURE P3-25

- 3-26 Use the superposition principle to find v_O in Figure P3-26.

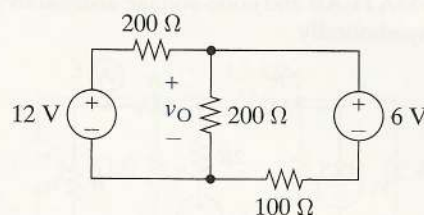


FIGURE P3-26

- 3-27 Use the superposition principle to find i_O in Figure P3-27. Verify your answer using OrCAD.

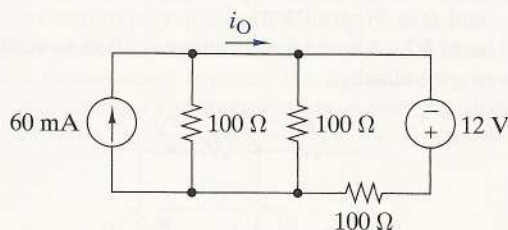


FIGURE P3-27

- 3-28 Use the superposition principle to find v_O in Figure P3-28.

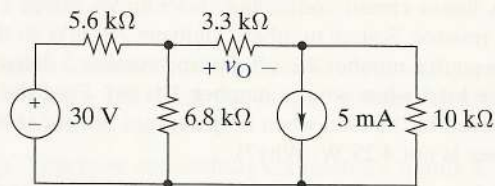


FIGURE P3-28

- 3-29 Use the superposition principle to find i_O in Figure P3-29. Verify your answer using OrCAD.

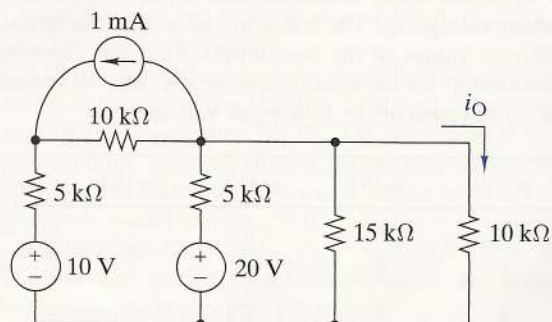


FIGURE P3-29

- 3-30(a)** Use the superposition principle to find v_O in terms of v_1 , v_2 , and R in Figure P3-30.
(b) Use MATLAB and node-voltage analysis to verify your answer symbolically.

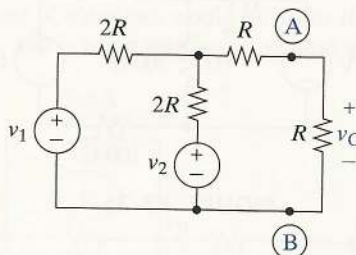


FIGURE P3-30

- 3-31(a)** Use the superposition principle to find v_O in terms of v_S , i_S , and R in Figure P3-31.
(b) Use MATLAB and node-voltage analysis to verify your answer symbolically.

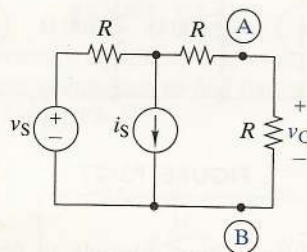


FIGURE P3-31

- 3-32** A linear circuit containing two sources drives a $100\text{-}\Omega$ load resistor. Source number 1 delivers 250 mW to the load when source number 2 is off. Source number 2 delivers 4 W to the load when source number 1 is off. Find the power delivered to the load when both sources are on. (Hint: The answer is not 4.25 W . Why?)
- 3-33** A linear circuit is driven by an independent voltage source $v_S = 10\text{ V}$ and an independent current source $i_S = 10\text{ mA}$. The output voltage is $v_O = 2\text{ V}$ when the voltage source is on and the current source off. The output is $v_O = 1\text{ V}$ when both sources are on. Find the output voltage when $v_S = 20\text{ V}$ and $i_S = -20\text{ mA}$.
- 3-34** A certain linear circuit has four input voltages and one output voltage v_O . The following table lists the output for different values of the four inputs. Find the input-output relationship for the circuit. Specifically, find an expression for v_O in terms of the four input voltages.

v_{S1} (V)	v_{S2} (V)	v_{S3} (V)	v_{S4} (V)	v_O (V)
2	4	-4	1	20
1	2	2	1.5	-4
1	4	2	2	-1
0	5	3	-1	3

OBJECTIVE 3-3 THÉVENIN EQUIVALENT CIRCUITS

Given a circuit containing sources,

- (a) Find the Thévenin or Norton equivalent circuit of terminals.
 (b) Use the Thévenin or Norton equivalent circuit to find the power delivered to linear or nonlinear load.
 See Examples 3-13, 3-14, 3-24, 3-25, 3-26

- 3-35(a)** Find the Thévenin equivalent circuit by R_L in Figure P3-35.
(b) Use the equivalent circuit to find the power delivered to $R_L = 47\text{ k}\Omega$.

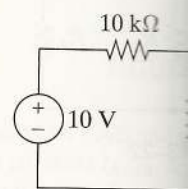


FIGURE P3-35

- 3-36(a)** Find the Thévenin equivalent circuit by R_L in Figure P3-36.
(b) Use the equivalent circuit to find the power delivered to R_L in terms of i_S , R_1 , R_2 , and R_L .
(c) Check your answer to (b) by finding the power delivered to R_L in the original circuit.

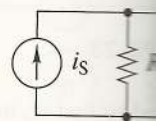


FIGURE P3-36

- 3-37** Find the Thévenin equivalent circuit by R_L in Figure P3-37. Find the voltage across R_L when $R_L = 10\text{ }\Omega$, and $50\text{ }\Omega$.

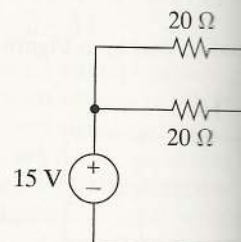


FIGURE P3-37

SUMMARY

- A linear dependent source generates a voltage or a current whose value is proportional to a voltage or current at another point in a circuit. There are four such sources: the current-controlled voltage source, the voltage-controlled voltage source, the current-controlled current source, and the voltage-controlled current source.
- Circuits containing dependent sources can be analyzed by node-voltage or mesh-current methods. Such circuits can have input-output relationships that produce voltage, current, or power gain. The presence of feedback can dramatically influence the input and output resistances of active circuits.
- The OP AMP is an active device with five terminals called the inverting input, the noninverting input, the output, and two power supply terminals. The device is a high-gain differential amplifier with three possible operating modes: +saturation, -saturation, and linear. The output predicted by the linear mode circuit

model is the actual
 • The ideal op amp has an infinite input resistance. The $i_N = 0$ approximation.
 • The four basic op amp configurations: inverting, noninverting, voltage follower, or design on these connections and the input of a
 • Important op amp applications: voltage-to-analog, current-to-analog, and comparators.

PROBLEMS

OBJECTIVE 4-1 LINEAR ACTIVE CIRCUITS (SECTS. 4-1, 4-2)

Given a circuit containing linear resistors, dependent sources, and independent sources, find selected output signal variables, input-output relationships, or input-output resistances. See Examples 4-1, 4-2, 4-3, 4-4, 4-5, 4-6, 4-7, 4-8, 4-9 and Exercises 4-1, 4-2, 4-3, 4-5, 4-6, 4-7, 4-8, 4-9, 4-10, 4-11

- 4-1 Find the voltage gain v_O/v_S and current gain i_O/i_x in Figure P4-1 for $r = 10 \text{ k}\Omega$.



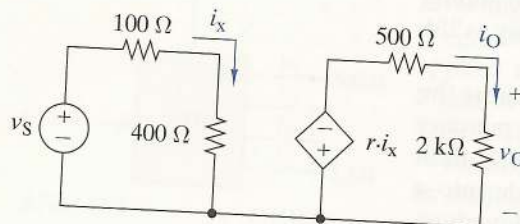


FIGURE P4-1

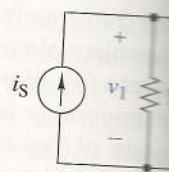- 4-2 Find the voltage gain v_O/v_1 and the current gain i_O/i_S in Figure P4-2. For $i_S = 2 \text{ mA}$, find the power supplied by the input current source and the power delivered to the $2\text{-k}\Omega$ load resistor.



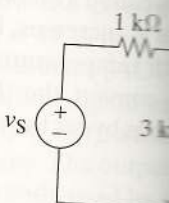- 4-3 Find the voltage gain v_O/v_1 in Figure P4-3.



- 4-4 (a) Find the voltage gain v_O/v_1 in Figure P4-4.

Verify your answers by simulating the circuit in OrCAD.

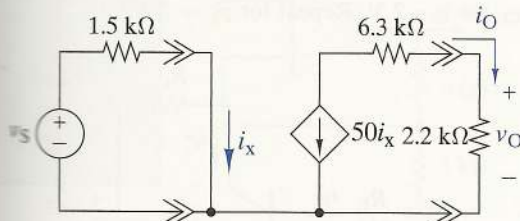


FIGURE P4-4

Find the voltage gain v_O/v_S in Figure P4-5.

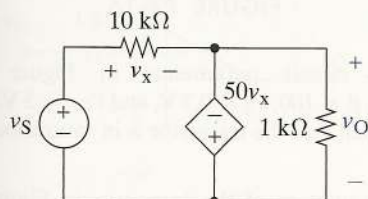


FIGURE P4-5

Find an expression for the current gain i_O/i_S in Figure P4-6. (Hint: Apply KCL at node A.)

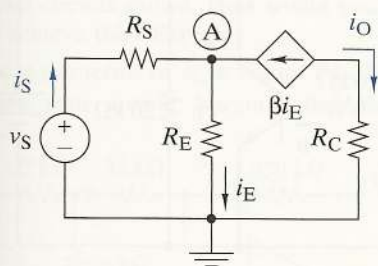


FIGURE P4-6

Find the voltage v_O in Figure P4-7.

Verify your answer by simulating the circuit in OrCAD.

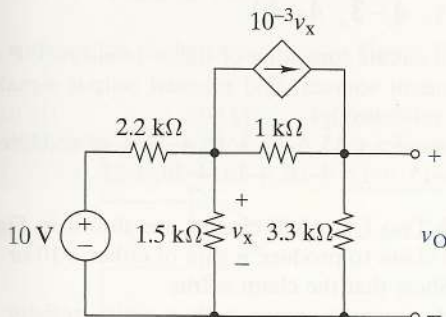


FIGURE P4-7

4-8 (a) Find an expression for the current gain i_O/i_S in Figure P4-8.

(b) Find an expression for the voltage gain v_O/v_S in Figure P4-8.

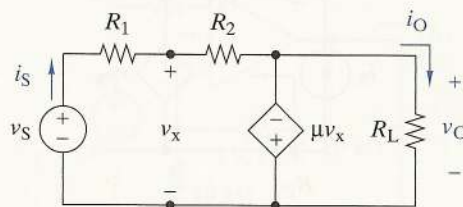


FIGURE P4-8

4-9 Find an expression for the voltage gain v_O/v_S in Figure P4-9.

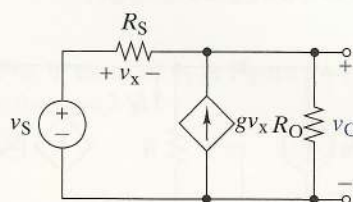


FIGURE P4-9

4-10 (a) Find an expression for the voltage gain v_O/v_S in Figure P4-10.

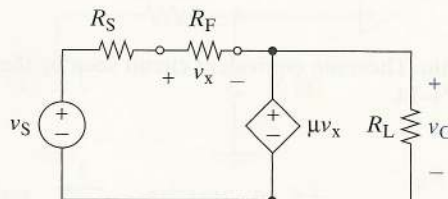


FIGURE P4-10

(b) Let $R_S = 10 \text{ k}\Omega$, $R_L = 10 \text{ k}\Omega$, and $\mu = 100$. Find the voltage gain v_O/v_S as a function of R_F . What is the voltage gain when R_F is an open circuit, when R_F is a short circuit, and for $R_F = 100 \Omega$?

(c) Simulate the circuit in OrCAD by varying R_F from 1Ω to $10 \text{ M}\Omega$. Read your output for $R_F = 100 \Omega$. How does your answer compare with that for part (b)?

4-11 Find the Thévenin equivalent circuit that the load R_L sees in Figure P4-11.

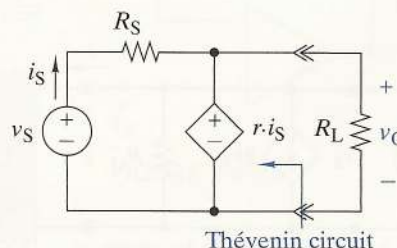


FIGURE P4-11