

4-12 Find R_{IN} in Figure P4-12.

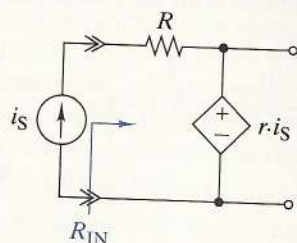


FIGURE P4-12

4-13 Find R_{IN} in Figure P4-13.

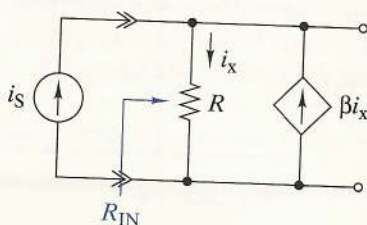


FIGURE P4-13

4-14 Find the Thévenin equivalent circuit seen by the load in Figure P4-14.

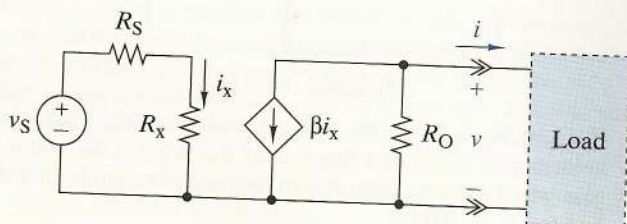


FIGURE P4-14

4-15 Find the Norton equivalent circuit seen by the load in Figure P4-15.

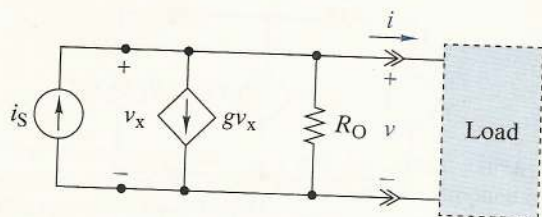


FIGURE P4-15

4-16 The circuit parameters in Figure P4-16 are $R_B = 4\text{ k}\Omega$, $\beta = 120$, $V_T = 0.7\text{ V}$, and $V_{CC} = 15\text{ V}$. Find i_C for $v_S = 2\text{ V}$. Repeat for $v_S = 5\text{ V}$.

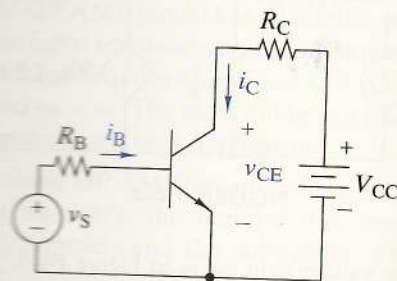


FIGURE P4-16

4-17 The circuit parameters in Figure P4-17 are $R_C = 3\text{ k}\Omega$, $\beta = 100$, $V_T = 0.7\text{ V}$, and $V_{CC} = 5\text{ V}$. Select R_B such that the transistor is in saturation mode $v_S \geq 2\text{ V}$.

4-18 The parameters of the transistor in Figure P4-18 are $\beta = 50$ and $V_T = 0.7\text{ V}$. Find i_C and v_{CE} for $v_S = 0.8\text{ V}$. Repeat for $v_S = 2\text{ V}$.

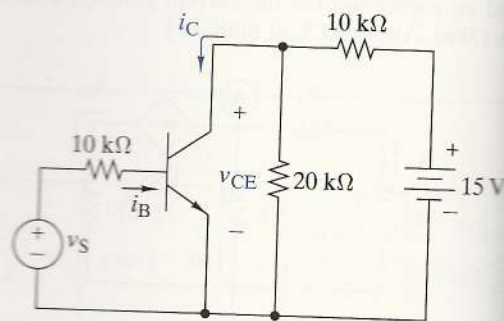


FIGURE P4-18

OBJECTIVE 4-2 OP AMP CIRCUIT ANALYSIS (SECTS. 4-3, 4-4)

Given a circuit consisting of linear resistors, OP AMPs, independent sources, find selected output signals or output relationships.

See Examples 4-13, 4-14, 4-16, 4-17, 4-18 and Exercises 4-14, 4-15, 4-17, 4-18, 4-19, 4-20, 4-21

4-19 Two OP AMP circuits are shown in Figure P4-19. Both claim to produce a gain of either $+10$ or -10 .

(a) Show that the claim is true.


(b) A practical source with a series resistor of $1\text{ k}\Omega$ connected to the input of each circuit. Does the claim still hold? If it does not, explain why.

are $R_B = 50 \text{ k}\Omega$, $V_S = 5 \text{ V}$. Find i_C and v_{CE} .

V_{CC}

Figure P4-16 and $V_S = 5 \text{ V}$. Select a value for R_B such that the transistor is in the active mode when $v_S = 0.8 \text{ V}$. Repeat for $v_S = 0.8 \text{ V}$.

Figure P4-18 and $V_S = 0.8 \text{ V}$. Repeat for $v_S = 0.8 \text{ V}$.

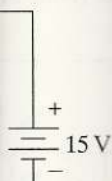

ANALYSIS

OP AMPs, and signals or inputs.

and Exercises 4-22.

in Figure P4-21, $v_S = 10 \text{ V}$ or -10 V .

resistor of $1 \text{ k}\Omega$. Does the original circuit satisfy the requirements?

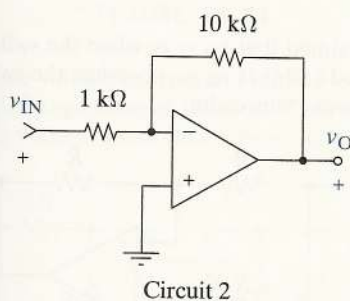
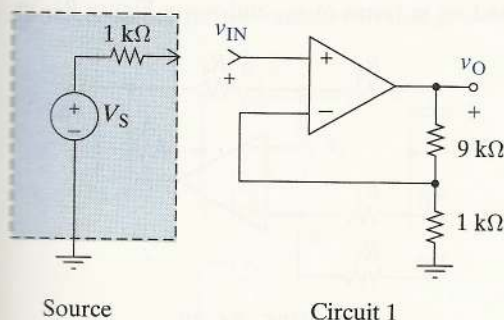


FIGURE P4-19

Suppose the output of the practical source shown in Figure P4-19 needs to be amplified by -100 and you can use only the two circuits shown. How would you connect the circuits to achieve this? Explain.

(a) Find v_O in terms of v_S in Figure P4-21.

(b) Validate your answer by simulating the circuit in SPICE.

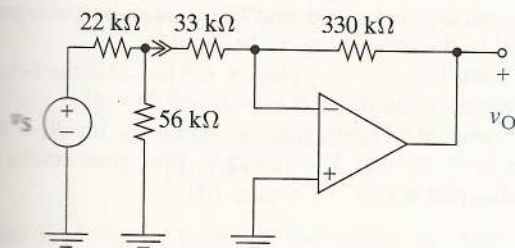


FIGURE P4-21

What is the range of the gain v_O/v_S in Figure P4-22?

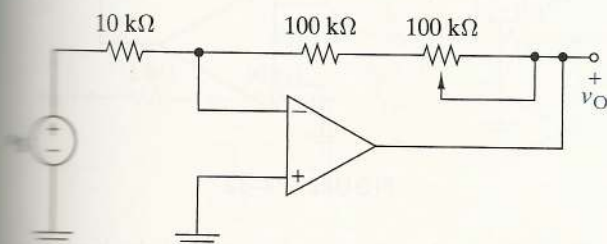


FIGURE P4-22

4-23 (a) Find v_O in terms of v_S in Figure P4-23.

(b) Find i_O for $v_S = 1 \text{ V}$. Repeat for $v_S = 3 \text{ V}$.

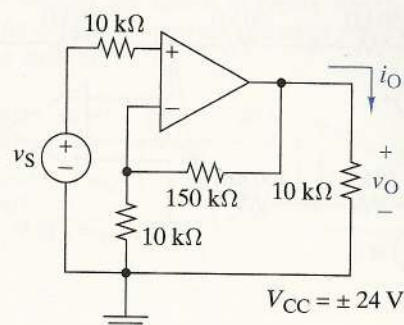


FIGURE P4-23

4-24 (a) Find v_O in terms of v_S in Figure P4-24.

(b) Find i_O for $v_S = 2 \text{ V}$.

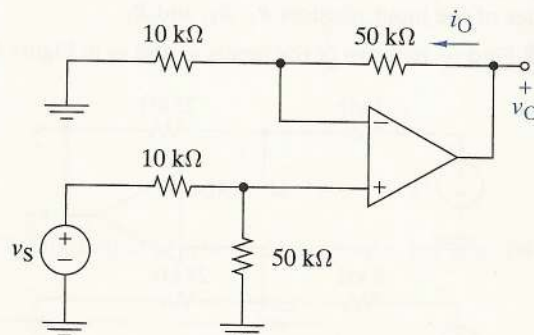


FIGURE P4-24

4-25 What is the gain v_O/v_S in Figure P4-25 when the switch is in position 1? Repeat for positions 2 and 3.

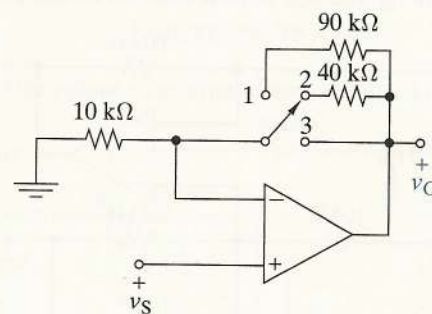


FIGURE P4-25

4-26 (a) Find v_O in terms of the inputs v_1 and v_2 in Figure P4-26.

- (b) If $v_1 = 1$ V, what is the range of values v_2 can have without saturating the OP AMP?

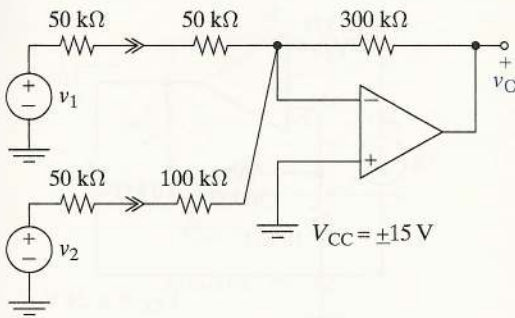


FIGURE P4-26

- 4-27 The input-output relationship for a three-input inverting summer is

$$v_O = -(v_1 + 10v_2 + 100v_3)$$

The resistance of the feedback resistor is 100 kΩ. Find the values of the input resistors R_1 , R_2 , and R_3 .

- 4-28 Find v_O in terms of the inputs v_1 and v_2 in Figure P4-28.

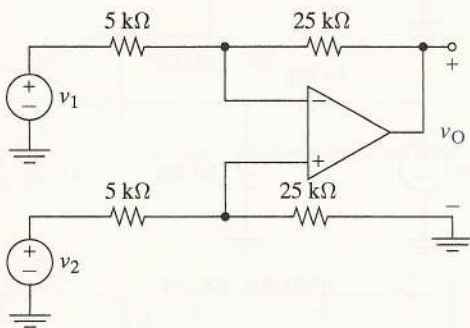


FIGURE P4-28

- 4-29 The switch in Figure P4-29 is open. Find v_O in terms of the inputs v_{S1} and v_{S2} . Repeat with the switch closed.

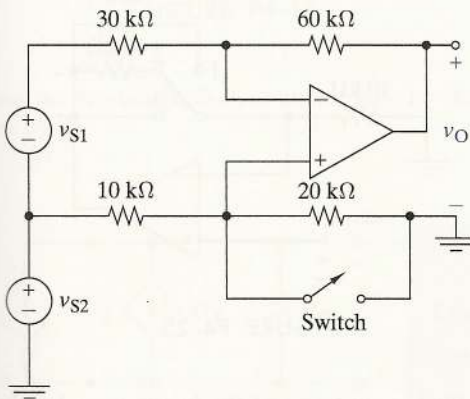


FIGURE P4-29

- 4-30 Find v_O in terms of v_{S1} and v_{S2} in Figure P4-30.

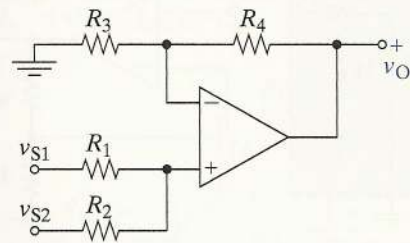


FIGURE P4-30

- 4-31 It is claimed that $v_O = v_S$ when the switch in Figure P4-31 is closed and that $v_O = -v_S$ when the switch is open. Prove or disprove this claim.

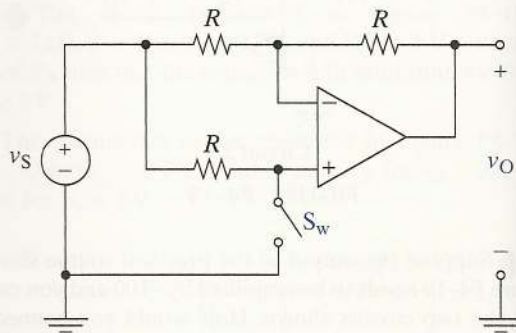


FIGURE P4-31

- 4-32 The circuit in Figure P4-32 has a diode in its feedback path and is called a "log amp" because its output is proportional to the natural log of the input.

(a) Show that $v_O = -V_T \ln(1 + v_S/(R_S I_O))$ if the $i-v$ characteristics of the diode is $i_D = I_O(e^{v_D/V_T} - 1)$.

(b) Using MATLAB, plot v_O versus v_S for $R_S = 10$ kΩ, $I_O = 10^{-14}$ A, and $V_T = 0.025$ V. Plot your results on a semilog plot for 10^{-6} V $\leq v_S \leq 100$ V.

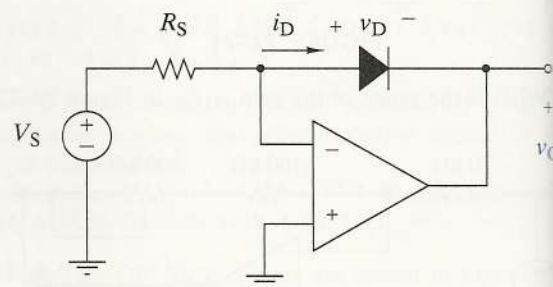


FIGURE P4-32

- 4-33 (a) Use node voltage analysis to find the input-output relationship or K of the circuit in Figure P4-33.

- 4-40 Find the output v_O in terms of the input v_1 in Figure P4-40. Verify your answer using OrCAD.

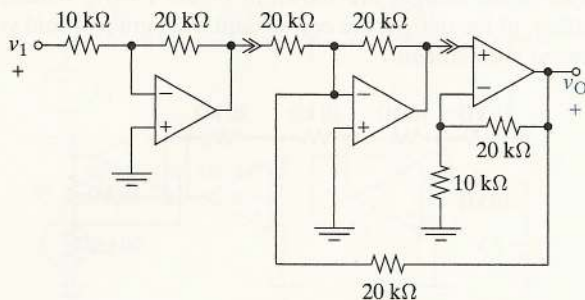


FIGURE P4-40

OBJECTIVE 4-3 OP AMP CIRCUIT DESIGN AND EVALUATION (SECT. 4-5)

Given an input-output relationship, use resistors and OP AMPs to design one or more circuits that implement the relationship within the stated constraints. Choose the better of two working circuits to meet certain constraints.

See Design Examples 4-12, 4-15, 4-20, 4-21, 4-22, 4-23, 4-24, Design Exercises 4-12, 4-16, 4-22, 4-28, 4-29, 4-30, Evaluation Examples 4-19, 4-20, 4-21, 4-22

- 4-41 Design an OP AMP amplifier with a voltage gain of -10 and an input resistance greater than $10\text{ k}\Omega$ using standard 5% resistance values less than $300\text{ k}\Omega$.
- 4-42 Design an OP AMP amplifier with a voltage gain of 4 using only $10\text{-k}\Omega$ resistors and one OP AMP.
- 4-43 Using a single OP AMP, design a circuit with inputs v_1 and v_2 and an output $v_O = 2v_2 - 3v_1$. The input resistance seen by each input should be greater than $5\text{ k}\Omega$.
- 4-44 Design a differential amplifier with inputs v_1 and v_2 and an output $v_O = 10(v_2 - v_1)$ using only one OP AMP. All resistances must be between $5\text{ k}\Omega$ and $200\text{ k}\Omega$.
- 4-45 Using no more than two OP AMPs, design an OP AMP circuit with inputs v_1 , v_2 , and v_3 and an output $v_O = -3v_1 + 2v_2 - 5v_3$.
- 4-46 Design the interface circuit in Figure P4-46 so that 10 mW is delivered to the $100\text{-}\Omega$ load. Repeat for a $100\text{-k}\Omega$ load. Verify your designs using OrCAD.

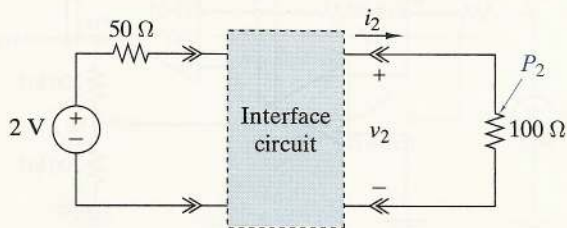


FIGURE P4-46

- 4-47 Design the interface circuit in Figure P4-47 so that the output is $v_2 = 150v_1 - 25$.

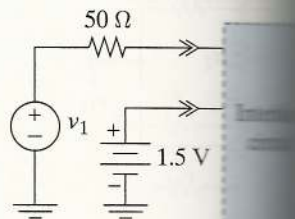


FIGURE P4-47

- 4-48 (a) Design a circuit that implements the input-output relationship $v_2 = 5v_1$ using two OP AMPs and standard 5% resistance values less than $300\text{ k}\Omega$.
(b) Repeat using only one OP AMP.
- 4-49 A requirement exists for a circuit that implements the input-output relationship $v_2 = 10v_1 - 5$. Design two different circuits that implement this relationship using one or more OP AMPs and standard 5% resistance values less than $300\text{ k}\Omega$.

Two proposed designs are shown in Figure P4-49. As a project engineer, you must select the best design for production. Which of the two designs is best for production and why? Justify your selection by performing the required functions.

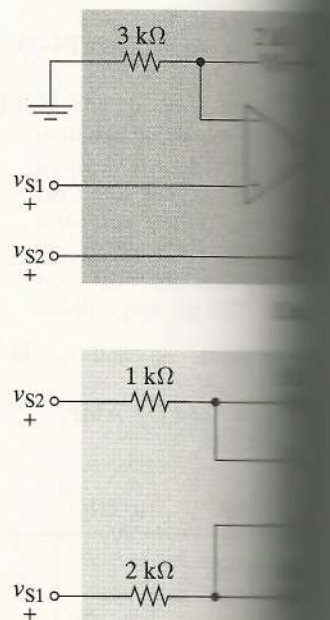


FIGURE P4-49


- 4-50 A requirement exists for a circuit that implements the input-output relationship $v_2 = 12v_1$. Design two different circuits that implement this relationship using one or more OP AMPs and standard 5% resistance values less than $300\text{ k}\Omega$.

in Figure P4-30.



30

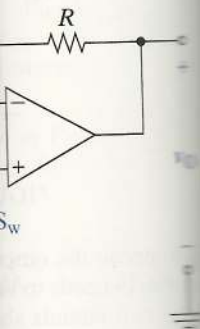when the switch is in position 1, the output is v_O . When the switch is in position 2, the output is v_O .



31

has a diode in its feedback path. Because its output is positive, the diode is forward-biased.

$v_S/(R_S I_O)$ if the diode is ideal. (e^{v_D/V_T} - 1). versus v_S for $R_S = 100 \text{ k}\Omega$. Plot your results for v_S from 0 to 100 V.

+ v_D -



4-32

analysis to find the input resistance at the input in Figure P4-33.

Select values for the resistors so that $K = -3$.

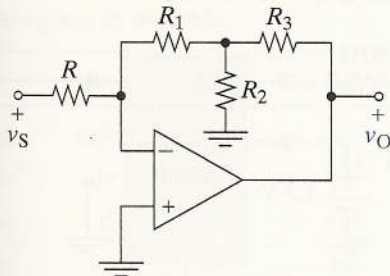


FIGURE P4-33

Use node voltage analysis in Figure P4-34 to show that $i_O = -v_S/2R$ regardless of the load. That is, show that the circuit is a voltage-controlled current source.

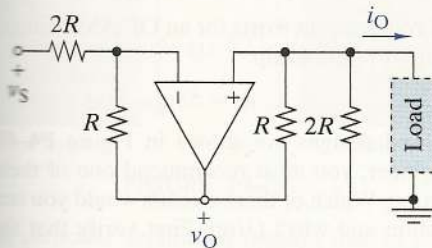


FIGURE P4-34

Find v_O in terms of the inputs v_{S1} and v_{S2} in Figure P4-35.

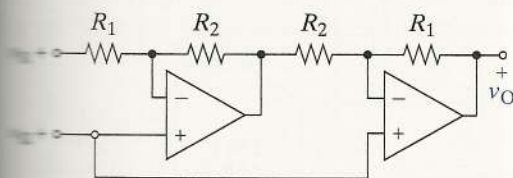


FIGURE P4-35

Find v_O in terms of the inputs v_{S1} and v_{S2} in Figure P4-36.

Redesign the circuit using only one OP AMP. Validate your design using OrCAD.



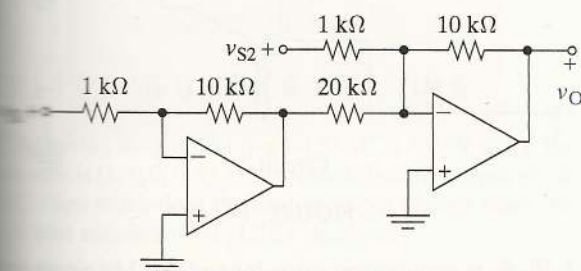


FIGURE P4-36

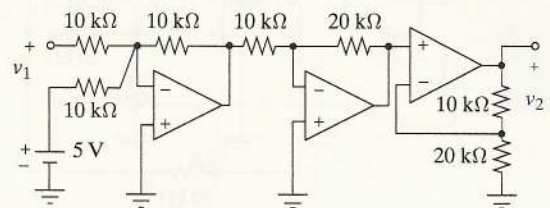4-37 On an exam, students were asked to design an efficient solution for the following relationship: $v_2 = 3v_1 + 15$. Two of the designs are shown in Figure P4-37. Which, if either, of the designs are correct and what grade would you award each student?



(a)

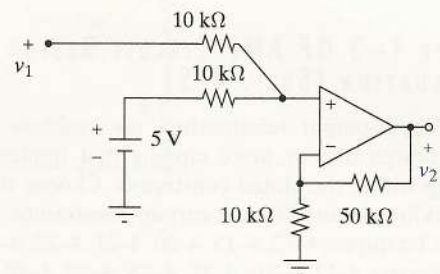

(b)

FIGURE P4-37

4-38 Find the output v_2 in terms of the input v_1 in Figure P4-38.

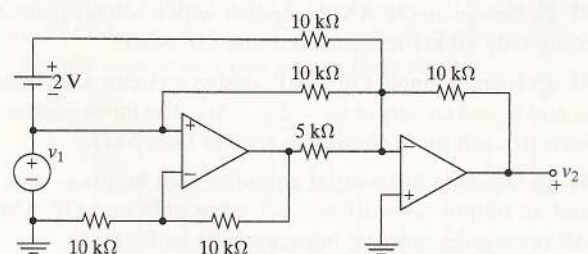


FIGURE P4-38

4-39 Find the output v_O in terms of the input v_S in Figure P4-39.

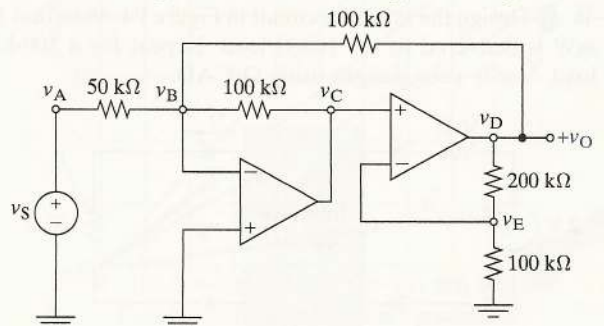


FIGURE P4-39