

1-13 The 12-V automobile battery in Figure P1-13 has an output capacity of 100 ampere-hours (Ah) when connected to a head lamp that absorbs 200 watts of power. Assume the battery voltage is constant.

- Find the current supplied by the battery.
- How long can the battery power the headlight?

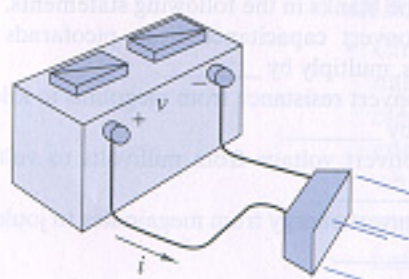


FIGURE P1-13

1-21 Two electrical devices are connected as shown in Figure P1-21. Using the reference marks shown in the figure, find the power transferred and state whether the power is transferred from A to B or B to A when

- $v = +33$ V and $i = -2.2$ A
- $v = -12$ V and $i = -1.2$ mA
- $v = +37.5$ V and $i = +40$ mA
- $v = -15$ V and $i = -43$ mA



FIGURE P1-21

1-24 Using the passive sign convention, the voltage across a device is $v(t) = 5 \cos(10t)$ V and the current through the device $i(t) = 0.5 \sin(10t)$ A. Calculate the device power at $t = 0.2$ s and $t = 0.4$ s and state whether the device is absorbing or delivering power.

1-2 A $6.2\text{-k}\Omega$ resistor dissipates 12 mW. Find the current through the resistor.

1-5 In Figure P2-5 find R_x and the power delivered to the resistor.

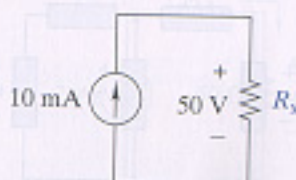


FIGURE P2-5

2-13 For the circuit in Figure P2-13:

- Identify the nodes and at least three loops in the circuit.
- Identify any elements connected in series or in parallel.
- Write KCL and KVL connection equations for the circuit.

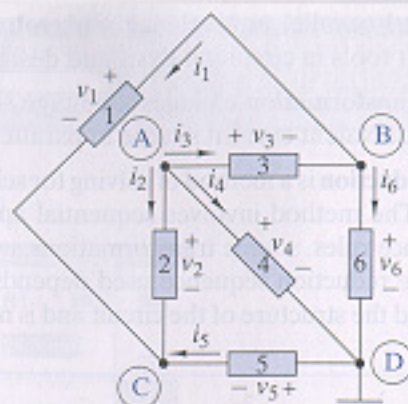


FIGURE P2-13

2-14 In Figure P2-13 $v_2 = 5$ V, $v_3 = -8$ V, and $v_4 = 3$ V. Find v_1 , v_5 , and v_6 .

2-20 Find v_x and i_x in Figure P2-20.

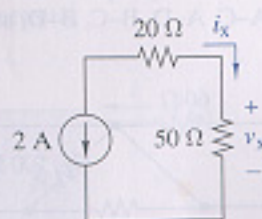


FIGURE P2-20

2-28 Find the equivalent resistance R_{EQ} in Figure P2-28.

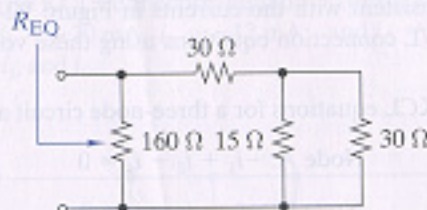


FIGURE P2-28

2-36 Select the value of R_x in Figure P2-36 so that $R_{EQ} = 60$ k Ω .

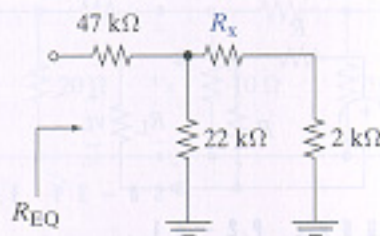


FIGURE P2-36