

- 2-42 Use current division in Figure P2-42 to obtain an expression for v_L in terms of R , R_L , and i_S .

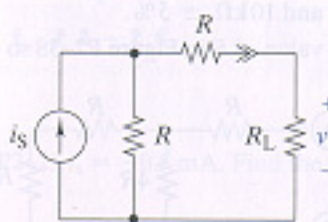


FIGURE P2-42

- 2-43 Find i_x in Figure P2-43.

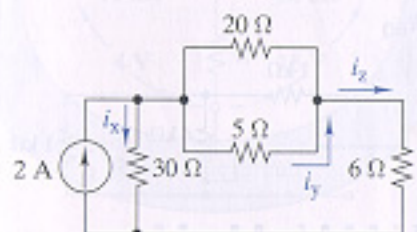


FIGURE P2-43

- 2-45 Find the range of values of v_O in Figure P2-45.

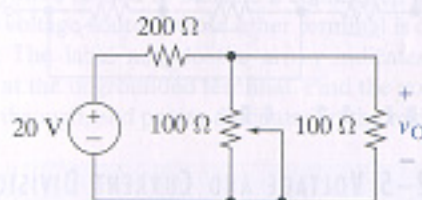


FIGURE P2-45

- 2-49 $\square$ Select a value of R_x in Figure P2-49 so that $v_L = 3$ V.

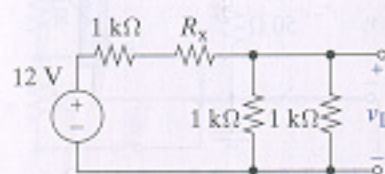


FIGURE P2-49

- 2-51 Use circuit reduction to find v_x and i_x in Figure P2-51.

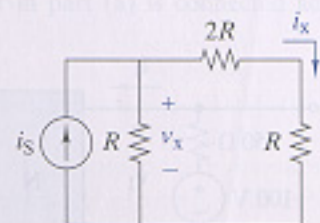


FIGURE P2-51

- 2-52 Use circuit reduction to find i_x in Figure P2-52.

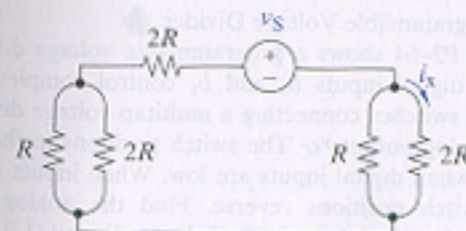


FIGURE P2-52

- 2-56 Use source transformation to find i_x in Figure P2-56.

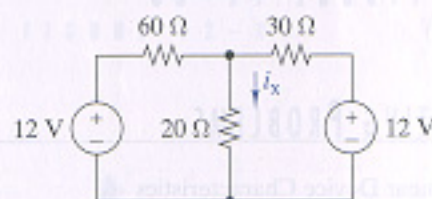


FIGURE P2-56

- 3-37 Find the Thévenin equivalent circuit seen by R_L in Figure P3-37. Find the voltage across the load when $R_L = 5 \Omega$, 10Ω , and 50Ω .

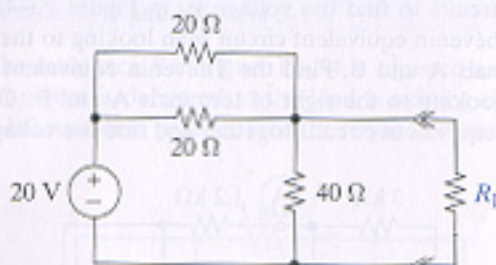


FIGURE P3-37

- 3-38 Find the Norton equivalent seen by R_L in Figure P3-38. Find the current through the load when $R_L = 6 \Omega$, 12Ω , and 60Ω .

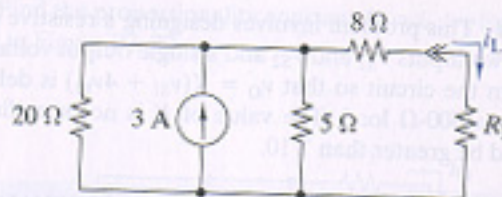


FIGURE P3-38

- 3-41 The purpose of this problem is to use Thévenin equivalent circuits to find the voltage v_x in Figure P3-41. Find the Thévenin equivalent circuit seen looking to the left of terminals A and B. Find the Thévenin equivalent circuit seen looking to the right of terminals A and B. Connect these equivalent circuits together and find the voltage v_x .

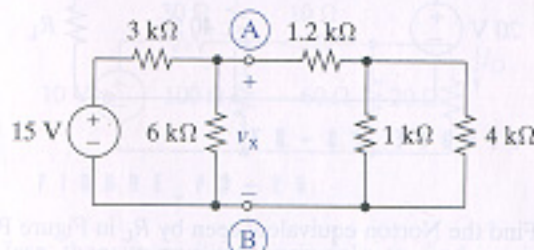


FIGURE P3-41