

3-9 (a) Formulate mesh-current equations for the circuit in Figure P3-9.

(b) Use these equations to find v_x and i_x .

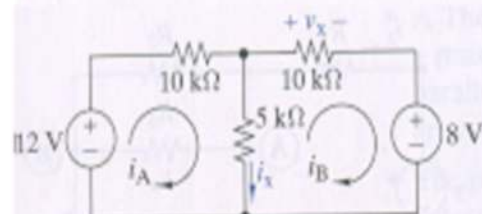


FIGURE P3-9

3-11 (a) Formulate mesh-current equations for the circuit in Figure P3-11.

(b) Use these equations to find v_x and i_x .

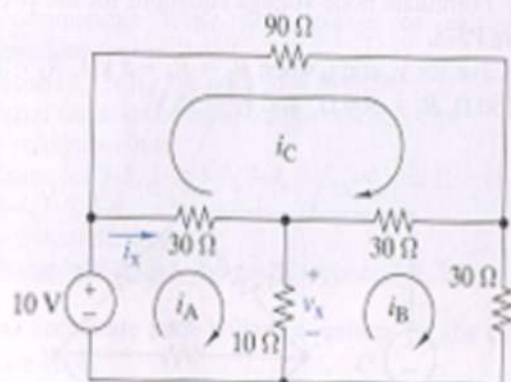


FIGURE P3-11

3-12 (a) Formulate mesh-current equations for the circuit in Figure P3-12.

(b) Solve for v_x and i_x when $R_1 = 200\Omega$, $R_2 = 300\Omega$, $R_3 = 50\Omega$, $R_4 = 250\Omega$, $R_5 = 200\Omega$, $i_s = 50\text{mA}$, and $v_s = 15\text{V}$.

(c) Find the total power dissipated in the circuit.

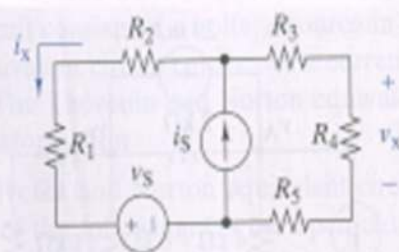


FIGURE P3-12

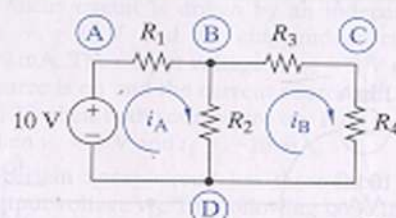


FIGURE P3-17

8 In Figure P3-17 all of the resistors are $1\text{ k}\Omega$. The voltage at node A is observed to be $v_A = 8\text{V}$ when node C is connected to ground. Find the node voltages v_B and v_D , and the mesh currents i_A and i_B .

3-27 Use the superposition principle to find i_O in Figure P3-27.

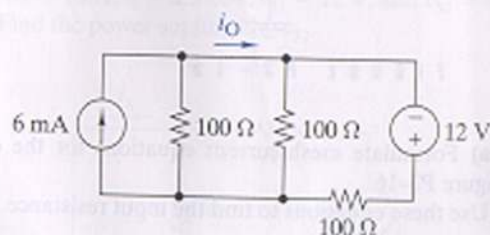


FIGURE P3-27

3-30 Use the superposition principle to find v_O in terms of v_1 , v_2 , and R in Figure P3-30.

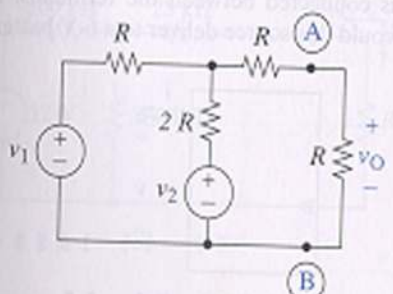


FIGURE P3-30

4-4 Find the voltage gain v_O/v_S and current gain i_O/i_x in Figure P4-4.

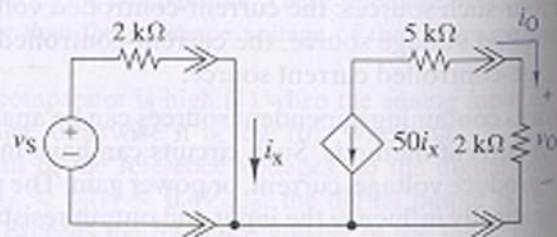


FIGURE P4-4

4-10 Find an expression for the voltage gain v_O/v_S in Figure P4-10.

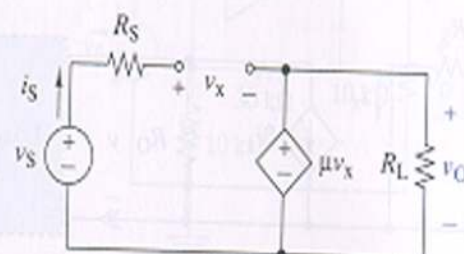


FIGURE P4-10

4-12 Find R_{IN} in Figure P4-12.

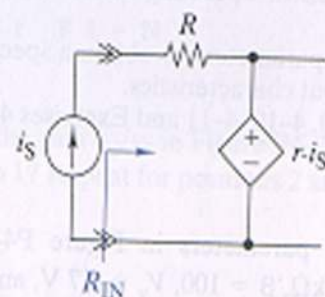


FIGURE P4-12

4-14 Find the Thévenin equivalent circuit seen by the load in Figure P4-14.

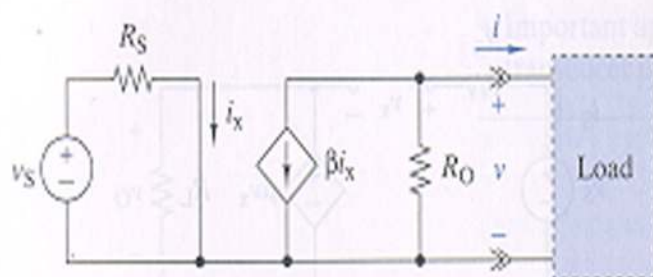


FIGURE P4-14