

4-21 Find v_O in terms of v_S in Figure P4-21.

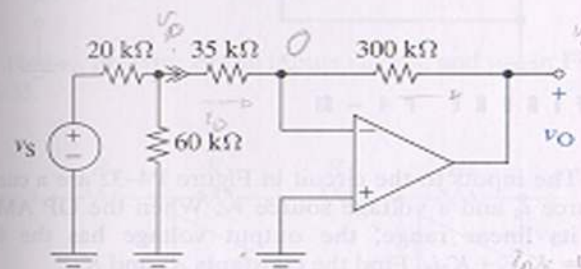


FIGURE P4-21

4-24 (a) Find v_O in terms of v_S in Figure P4-24.

(b) Find i_O for $v_S = 2$ V.

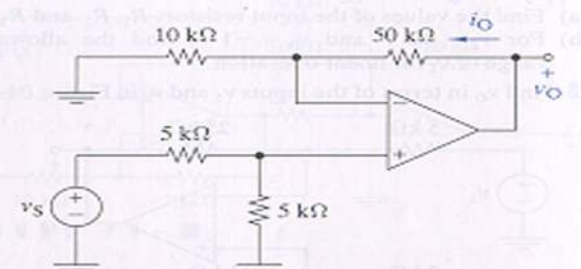


FIGURE P4-24

4-28 Find v_O in terms of the inputs v_1 and v_2 in Figure P4-28.

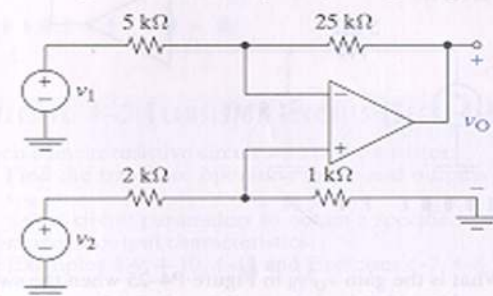


FIGURE P4-28

4-29 Find v_O in terms of the inputs v_{S1} and v_{S2} in Figure P4-29.

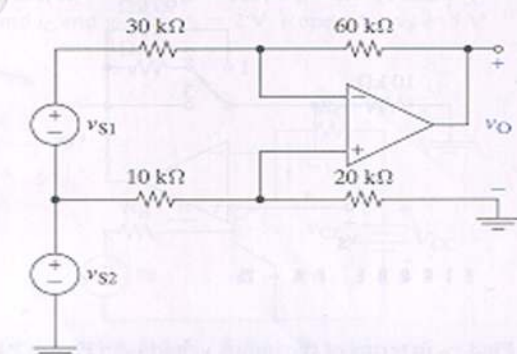


FIGURE P4-29

4-31 It is claimed that $v_O = v_S$ when the switch is closed in Figure P4-31 and that $v_O = -v_S$ when the switch is open. Prove or disprove this claim.

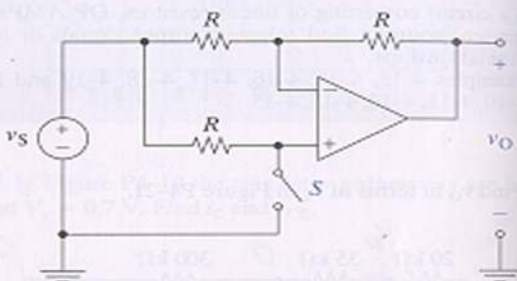


FIGURE P4-31

4-32 The inputs to the circuit in Figure P4-32 are a current source i_S and a voltage source v_S . When the OP AMP is in its linear range, the output voltage has the form $v_O = K_1 v_S + K_2 i_S$. Find the constants K_1 and K_2 .

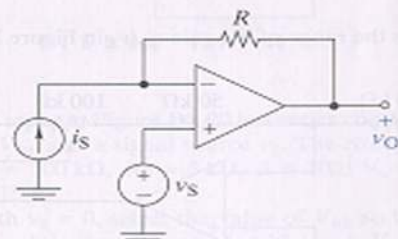


FIGURE P4-32

4-35 Find v_O in terms of the inputs v_{S1} , v_{S2} , and v_{S3} in Figure P4-35.

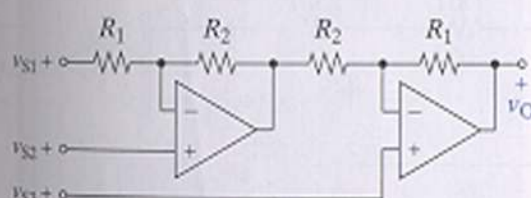


FIGURE P4-35

4-38 Find the output v_2 in terms of the input v_1 in Figure P4-38.

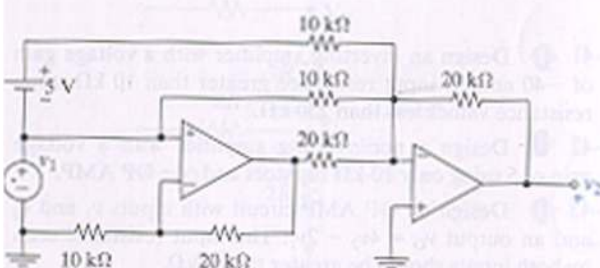


FIGURE P4-38

4-45 Using no more than two OP AMPs, design an OP AMP circuit with inputs v_1 , v_2 , and v_3 and an output $v_O = 3v_1 - 2v_2 - 5v_3$.

4-54 The output voltage of a semiconductor temperature sensor is $v_S = (10T + 500)$ mV, where T is the temperature in $^{\circ}\text{C}$. The sensor is to be used to measure temperatures in the range -40°C to 110°C . Design an interface circuit that translates this temperature range to a 0-V to 3-V output voltage range. Use a standard 5-V reference source to obtain any required bias voltage.