

HW#1; Problems Statement:

- 1-14 An incandescent lamp absorbs 100 W when connected to a 120-V source. A energy-efficient compact fluorescent lamp (CFL) producing the same amount of light absorbs 16 W when connected to the same source.

How much cheaper is it to operate the CFL versus the incandescent bulb over 1,000 hours when electricity costs 7.8 cents/kWh?

- 1-16 A string of holiday lights is protected by a 5-A fuse and has 25 bulbs, each of which is rated at 7 W. How many strings can be connected end-to-end across a 120 V circuit without blowing a fuse?

- 1-22 Figure P1-22 shows an electric circuit with a voltage and a current variable assigned to each of the six devices. The device voltages and currents are observed to be

	v (V)	i (A)		v (V)	i (A)
Device 1	15	-1	Device 4	-10	-1
Device 2	5	1	Device 5	20	-3
Device 3	10	2	Device 6	20	2

Find the power associated with each device and state whether the device is absorbing or delivering power. Use the power balance to check your work.

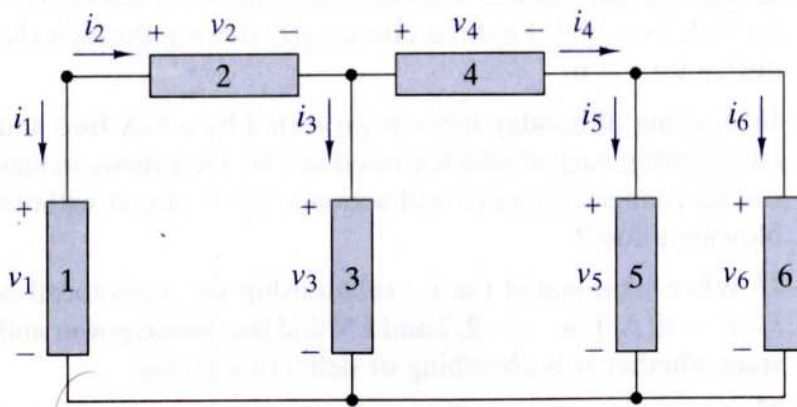


FIGURE P1-22

- 2-1 The current through a 56-k Ω resistor is 2.2 mA. Find the voltage across the resistor.

2-6 In Figure P2-6 find R_x and the power delivered to the resistor.

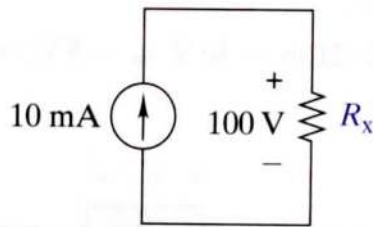


FIGURE P2-6

2-9 A 100-k Ω resistor has a power rating of 0.125 W. Find the maximum voltage that can be applied to the resistor.

2-12 A thermistor is a temperature-sensing element composed of a semiconductor material that exhibits a large change in resistance proportional to a small change in temperature. A particular thermistor has a resistance of 5 k Ω at 25 $^{\circ}\text{C}$. Its resistance is 340 Ω at 100 $^{\circ}\text{C}$. Assuming a straight-line relationship between these two values, at what temperature will the thermistor's resistance equal 1 k Ω ?

2-15 For the circuit in Figure P2-15:

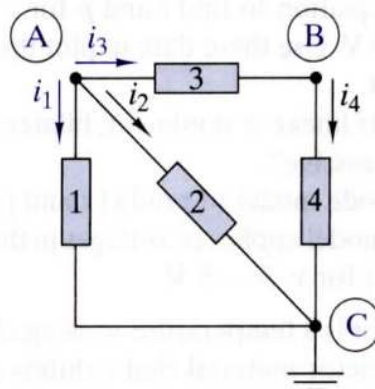


FIGURE P2-15

- Identify the nodes and at least two loops.
- Identify any elements connected in series or in parallel.
- Write KCL and KVL connection equations for the circuit.

2-20 The circuit in Figure P2-20 is organized around the three signal lines A, B, and C.

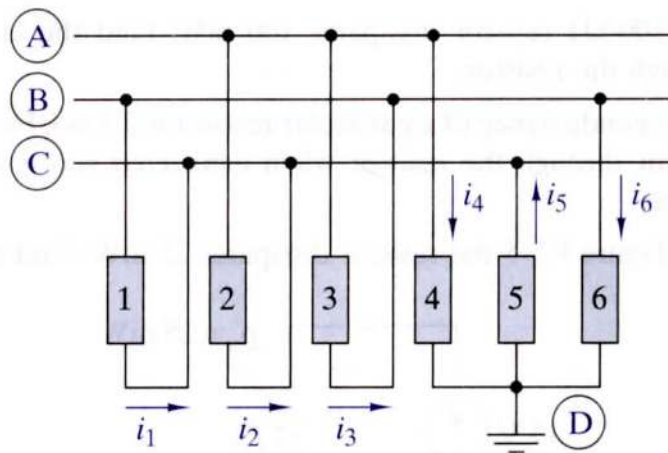


FIGURE P2-20

- Identify the nodes and at least three loops in the circuit.
- Write KCL connection equations for the circuit.
- If $i_1 = -20$ mA, $i_2 = -12$ mA, and $i_3 = 50$ mA, find i_4 , i_5 , and i_6 .
- Show that the circuit in Figure P2-20 is identical to that in Figure P2-17.

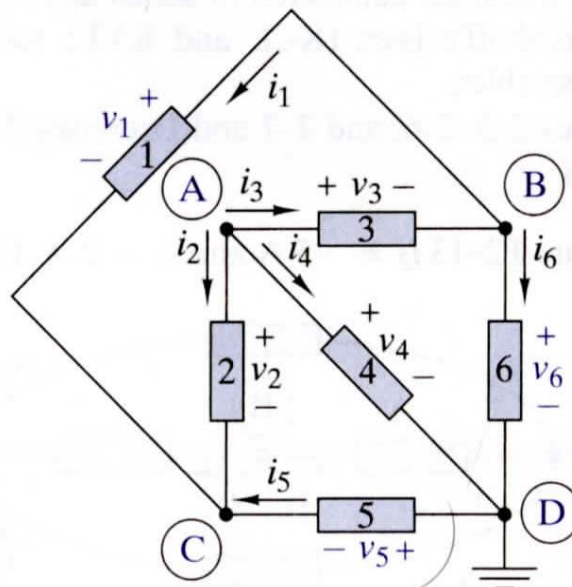


FIGURE P2-17

2-22 In Figure P2-22 $i_1 = 25$ mA, $i_2 = 10$ mA, and $i_3 = -15$ mA. Find i_4 and i_5 .

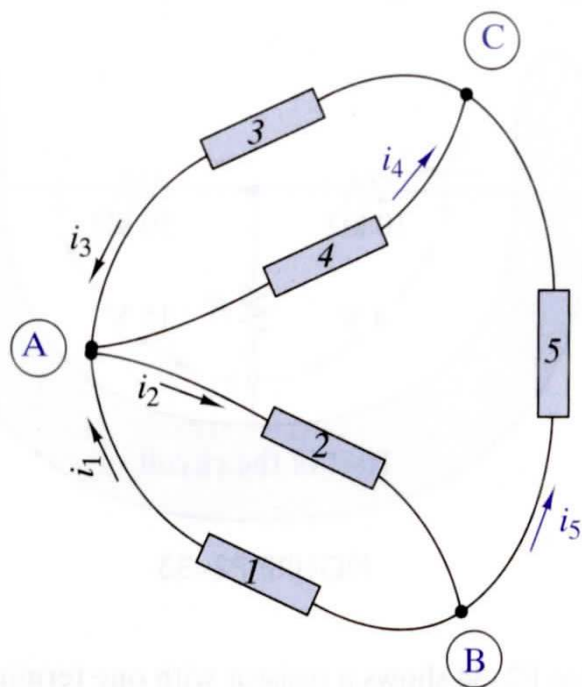


FIGURE P2-22