

HW#2

MAE 140

Winter 2014

2-25 Find v_x and i_x in Figure P2-25.

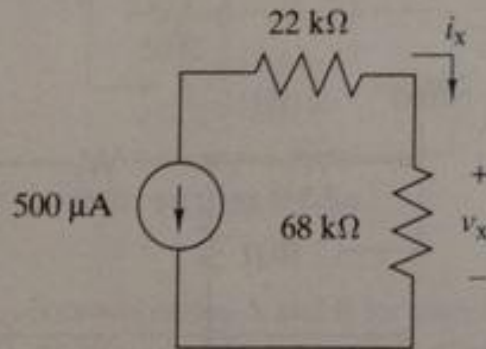


FIGURE P2-25

2-28 A modeler wants to light his model building using miniature grain-of-wheat light bulbs connected in parallel as shown in Figure P2-28. He uses two 1.5-V “C-cells” to power his lights. He wants to use as many lights as possible, but wants to limit his current drain to $500\ \mu\text{A}$ to preserve the batteries. If each light has a resistance of $36\ \text{k}\Omega$, how many lights can he install and still be under his current limit?

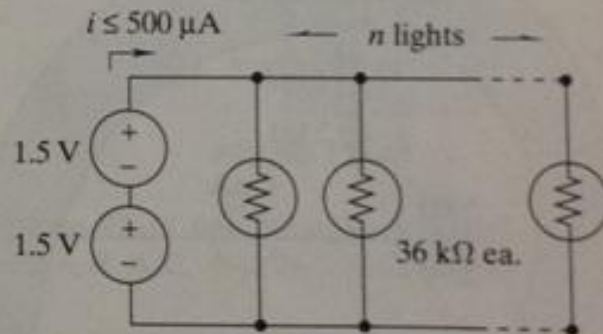


FIGURE P2-28

2-32 Figure P2-32 shows a subcircuit connected to the rest of the circuit at four points.

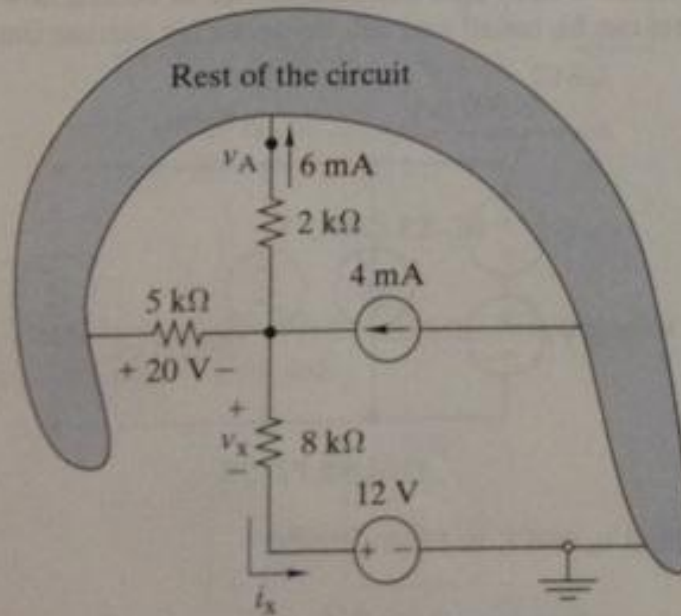


FIGURE P2-32

- (a) Use element and connection constraints to find v_x and i_x .
- (b) Show that the sum of the currents into the rest of the circuit is zero.
- (c) Find the voltage v_A with respect to the ground in the circuit.

2-36 Find the equivalent resistance R_{EQ} in Figure P2-36.

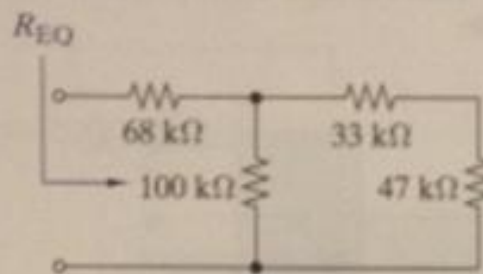


FIGURE P2-36

2-38 Equivalent resistance is defined at a particular pair of terminals. In the following figure the same circuit is looked at from two different terminal pairs. Find the equivalent resistances R_{EQ1} and R_{EQ2} in Figure P2-38. Note that in calculating R_{EQ2} the $33\text{-k}\Omega$ resistor is connected to an open circuit and therefore doesn't affect the calculation.

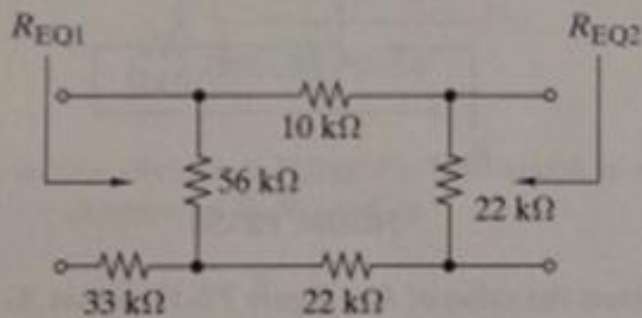


FIGURE P2-38

2-43 In Figure P2-43 find the equivalent resistance between terminals A-B, A-C, A-D, B-C, B-D, and C-D.

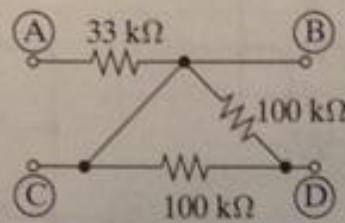


FIGURE P2-43

2-55 Use voltage division in Figure P2-55 to obtain an expression for v_L in terms of R , R_L , and v_S .

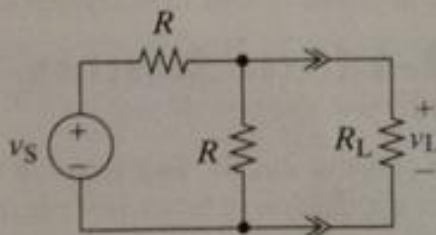


FIGURE P2-55

- 2-60 **A** The $1\text{-k}\Omega$ load in Figure P2-60 needs 5 V across it to operate correctly. Where should the wiper on the potentiometer be set (R_x) to obtain the desired output voltage?

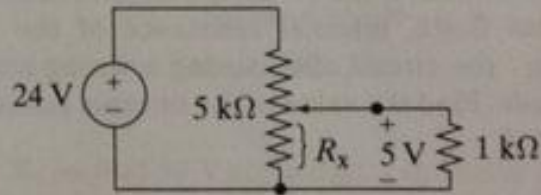


FIGURE P2-60

- 2-70 Use circuit reduction to find v_x and i_x in Figure P2-70.

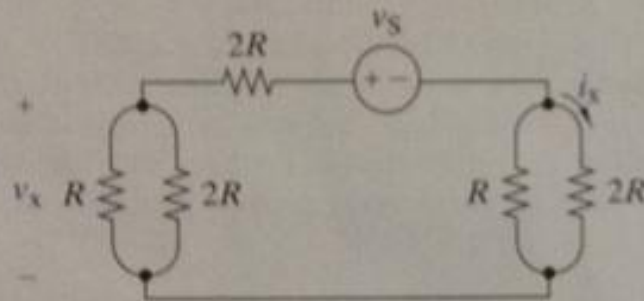


FIGURE P2-70

- 2-73 Use source transformation to find i_x in Figure P2-73.

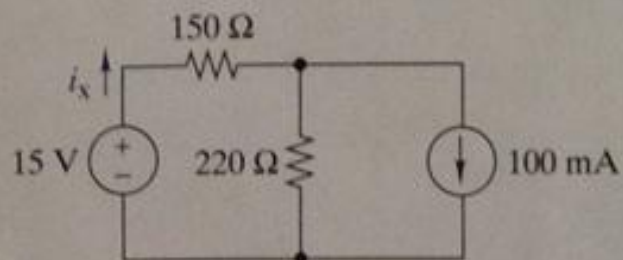


FIGURE P2-73