

HW#4; Problems Statement:

- 3-13(a)** Formulate mesh-current equations for the circuit in Figure P3-13. Arrange the results in matrix form $\mathbf{Ax} = \mathbf{b}$.
(b) Solve for i_A and i_B .
(c) Use these results to find v_x and i_x .

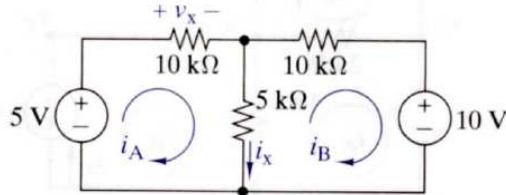


FIGURE P3-13

- 3-14(a)** Formulate mesh-current equations for the circuit in Figure P3-14. Arrange the results in matrix form $\mathbf{Ax} = \mathbf{b}$.
(b) Solve for i_A , i_B and i_C .
(c) Use these results to find v_x and i_x .

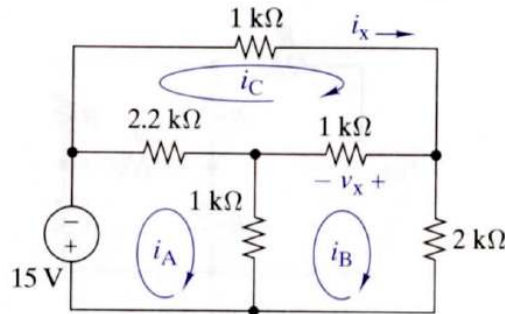


FIGURE P3-14

- 3-5 (a)** Formulate node-voltage equations for the circuit in Figure P3-5. Arrange the results in matrix form $\mathbf{Ax} = \mathbf{b}$.
(b) Solve these equations for v_A and v_C .
(c) Use these results to find v_x and i_x .

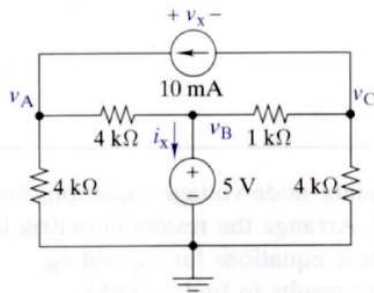


FIGURE P3-5

- 3-5 (a)** Formulate node-voltage equations for the circuit in Figure P3-5. Arrange the results in matrix form $\mathbf{Ax} = \mathbf{b}$.
(b) Solve these equations for v_A and v_C .
(c) Use these results to find v_x and i_x .

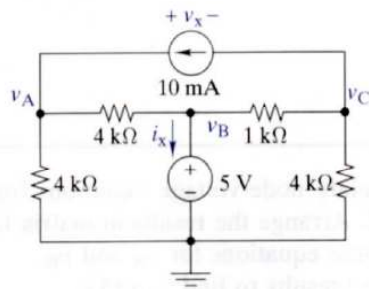


FIGURE P3-5

- 3-6 (a)** Choose a ground wisely and formulate node-voltage equations for the circuit in Figure P3-6.
(b) Solve for v_x and i_x when $R_1 = R_2 = R_3 = R_4 = 10 \text{ k}\Omega$, $v_s = 25 \text{ V}$, and $i_s = 1 \text{ mA}$.

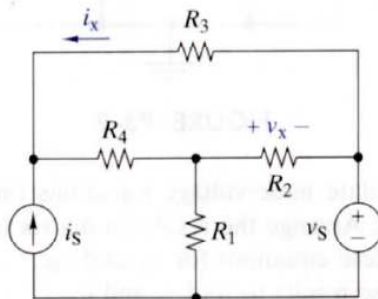


FIGURE P3-6

- 3-15(a)** Formulate mesh-current equations for the circuit in Figure P3-15. Arrange the results in matrix form $\mathbf{Ax} = \mathbf{b}$.
(b) Solve for i_A and i_B .
(c) Use these results to find v_x and i_x .

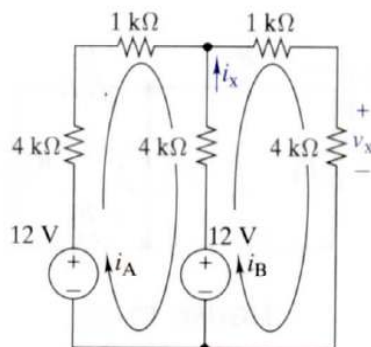


FIGURE P3-15

- 3-26(a)** Formulate mesh-current equations for the circuit in Figure P3-26.
- (b)** Formulate node-voltage equations for the circuit in Figure P3-26.
- (c)** Which set of equations would be easier to solve? Why?
- (d)** Use OrCAD to find the node voltages v_A and v_B and the mesh-currents i_A , i_B and i_C in Figure P3-26.

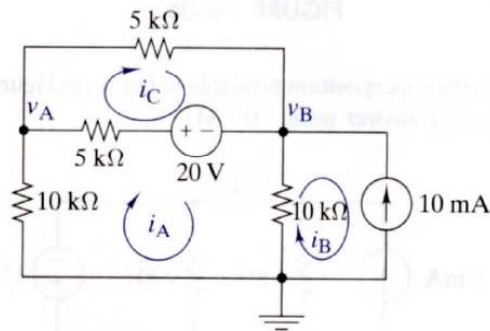


FIGURE P3-26

- 3-27(a)** Formulate mesh-current equations for the circuit in Figure P3-27. Arrange the results in matrix form $\mathbf{Ax} = \mathbf{b}$.
- (b)** Use MATLAB and mesh-current analysis to solve for the mesh currents i_A , i_B , i_C , and i_D in Figure P3-27.
- (c)** Formulate node-voltage equations for the circuit in Figure P3-27. Arrange the results in matrix form $\mathbf{Ax} = \mathbf{b}$.
- (d)** Use MATLAB and node-voltage analysis to solve for the mesh currents i_A , i_B , i_C , and i_D in Figure P3-27 and compare the effort required with each technique, i.e. mesh-current versus node-voltage.
- (e)** Use OrCAD to verify your results in the previous two parts.

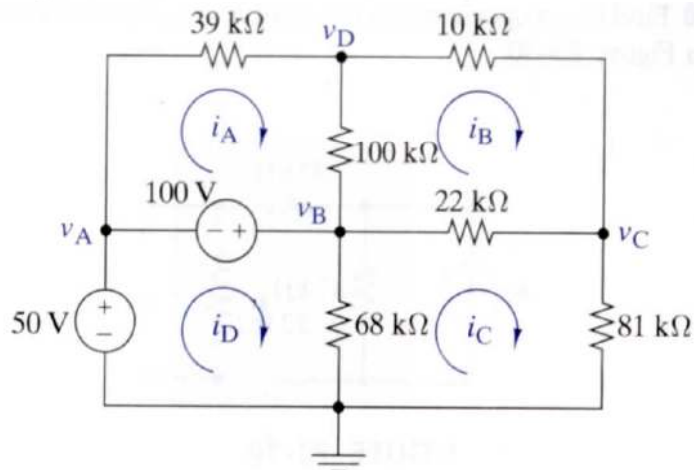


FIGURE P3-27

3-91 Audio Speaker Resistance-Matching Network

A company is producing an interface network that they claim would result in an R_{IN} of $600\ \Omega \pm 2\%$ and R_{OUT} of 16, 8, or $4\ \Omega \pm 2\%$ – depending on whether the connected speakers are 16, 8, or $4\ \Omega$ – selectable via a built-in switch. Their design is shown in Figure P3-91. Prove or disprove their claim.

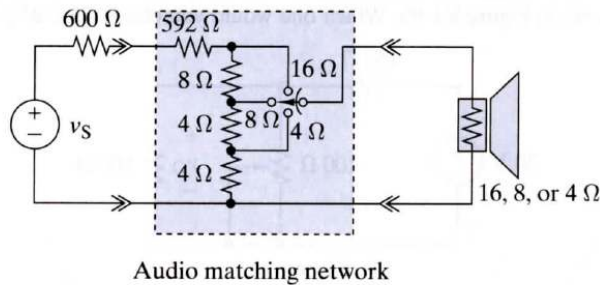


FIGURE P3-91

3-94 Battery Design

A satellite requires a battery with an open-circuit voltage $v_{OC} = 36\text{ V}$ and a Thévenin resistance $R_T \leq 10\ \Omega$. The battery is to be constructed using series and parallel combinations of one of two types of cells. The first type has $v_{OC} = 9\text{ V}$, $R_T = 4\ \Omega$, and a weight of 30 grams. The second type has $v_{OC} = 4\text{ V}$, $R_T = 2\ \Omega$, and a weight of 18 grams. Design a minimum weight battery that meets the open-circuit voltage and Thévenin resistance requirements.

3-95 Design Evaluation

A requirement exists for a circuit to deliver 0 to 5 V to a $100\text{-}\Omega$ load from a 20-V source rated at 2.5 W . Two proposed circuits are shown in Figure P3-95. Which one would you choose and why?

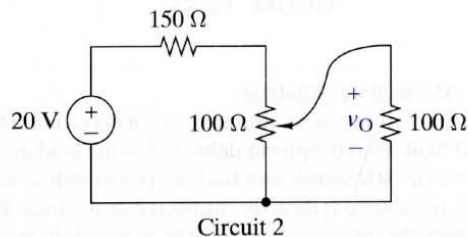
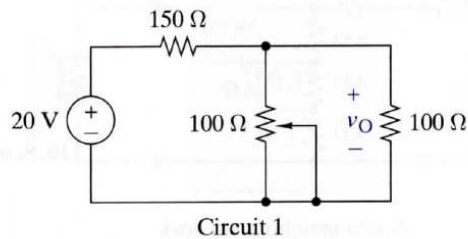


FIGURE P3-95